

Verilog introduction

Embedded and Ambient Systems Lab

Purpose of HDL languages


- Modeling hardware behavior
 - Large part of these languages can only be used for simulation, not for hardware generation (synthesis)
 - Synthesizable part depends on the actual synthesizer
- Replace graphical, schematic based design method (which very time consuming)
- RTL (Register Transfer Level) level description
 - Automatic hardware synthesis
 - Increase productivity

HDL languages

- Modular languages
- HDL module
 - Input and output port definitions
 - Logic equations between the inputs and the outputs
- Unlike software programming languages, NOT a sequential language
 - Describes PARALLEL OPERATIONS

Modules

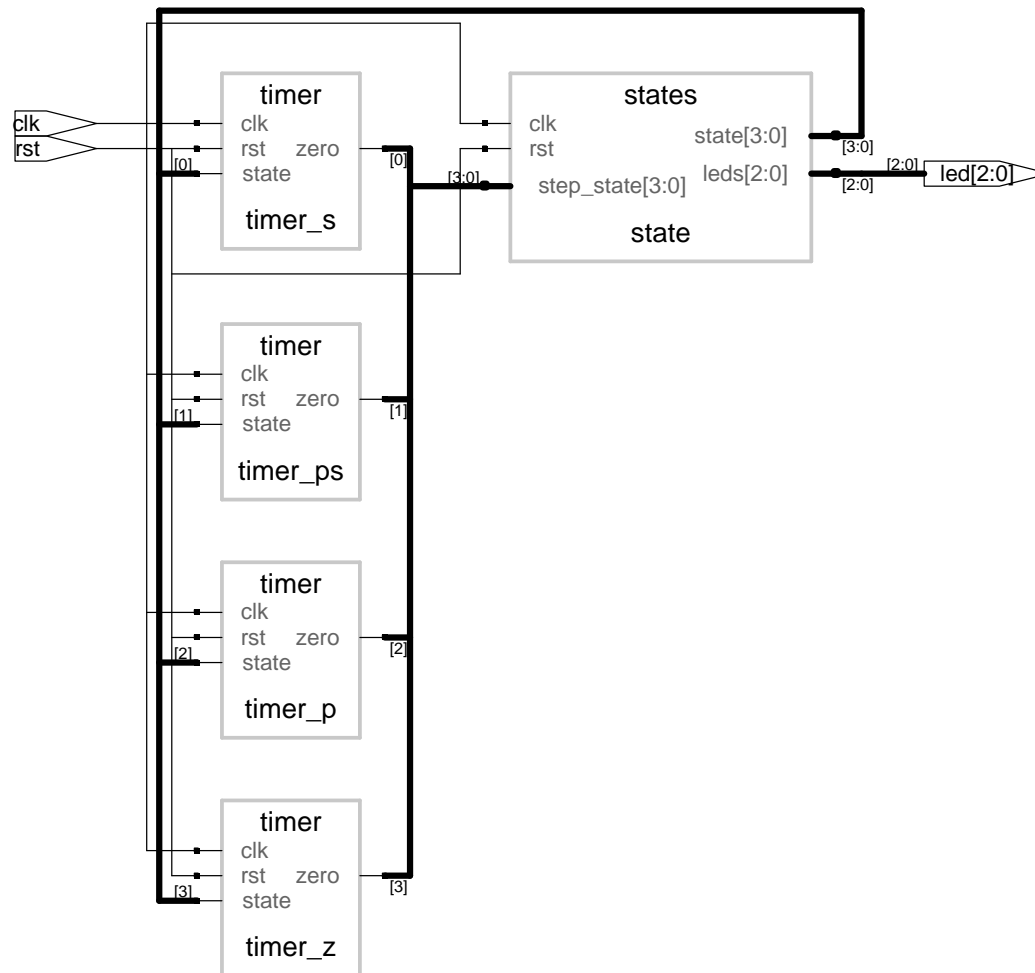- Building blocks to design complex, hierarchical systems
- Hierarchical description, partitioning



Verilog: module (2001)

„module” keyword

„module” name

```
module test(  
    input clk,  
    input [7:0] data_in,  
    output [7:0] data_out,  
    output reg valid  
);  
.....  
.....  
.....  
endmodule
```

Input ports

Output ports

„endmodule”
keyword

Functional
description

Verilog Syntax

- Comments (like C)
 - // one line
 - /* */ multiple lines
- Constants
 - <bit width><'base><value>
 - 5'b00100: 00100 decimal value: 4, 5 bit wide
 - 8'h4e: 01001110 decimal value: 78, 8 bit wide
 - 4'bZ: ZZZZ high impedance state

Bit operations

- \sim , $\&$, $|$, \wedge , $\sim\wedge$ (negate, and, or, xor, xnor)
- Bitwise operator on vectors, e.g.:
 - $4'b1101 \& 4'b0110 = 4'b0100$
- If the operand widths are not equal, the smaller one is extended with zeros
 - $2'b11 \& 4'b1101 = 4'b0001$
- (Logic operators: $!$, $\&\&$, $||$)

Bit reduction operators

- Operates on all bits of a vector, the output is a single bit
- $\&$, $\sim\&$, $|$, $\sim|$, \wedge , $\sim\wedge$ (and, nand, or, nor, xor, xnor)
 - $\&4'b1101 = 1'b0$
 - $|4'b1101 = 1'b1$
 - Typical usage scenarios:
 - Parity check

Comparison

- Same as in C
- Equal, not-equal
 - `==, !=`
 - `===`: equality considering „Z“, „X“
 - `!==`: not-equal considering „Z“, „X“
- Comparison
 - `<, >, <=, >=`

Arithmetic

- Same as in C
- Operators: $+$, $-$, $*$, $/$, $\%$
 - Not all of them is synthesizable
 - Typically division, modulo are only synthesizable when the second operator is power of 2
 - Negative numbers in twos-complement code

Other operators


- Concatenate: `{}`
E.g.:
 - `{4'b0101, 4'b1110} = 8'b01011110`
- Shift:
 - `<<, >>`
- Bit selection
 - Selected part has to be constant
 - `data[5:3]`

Data types

- wire
 - Behaves like a real wire (combinatorial logic)
 - Declaration of an 8 bit wire: `wire [7:0] data;`
- reg
 - After synthesis it can translate into
 - Wire
 - Latch
 - Flip-flop
 - E.g.: `reg [7:0] data;`

Assign

 
- **Assign** can be used only on **wire** types
- Continuous assignment
 - Left operand continuously gets a new value
- E.g.
 - assign c = a & b;



- A wire can be driven by only one **assign** statement
- Multiple **assigns** operate parallel to each other
- Can be used to describe combinatorial logic

Always block

- Syntax:

 

- A reg type variable should be written only in one **always** block
- The sensitivity list cannot contain the outputs (left-side variables) of the **always** block
- **Assign** cannot be used within an **always** block
- Multiple **always** blocks are executed in parallel


Always – assignments

- Blocking: =
 - Blocks the execution of operations after it till it is executed -> sequential operation (don't use it unless really necessary)
- Nonblocking: <=
 - Nonblocking assignments are executed in parallel -> hardware-like operation
- **Always use nonblocking assignment**

Always – Flip Flop


- Flip Flop: edge sensitive storage element
 
```
always @ (posedge clk)
    c <= a & b;
```




- Synchronous reset
 
```
always @ (posedge clk)
if (rst)
    c <= 1'b0;
else
    c <= a & b;
```



- Asynchronous reset

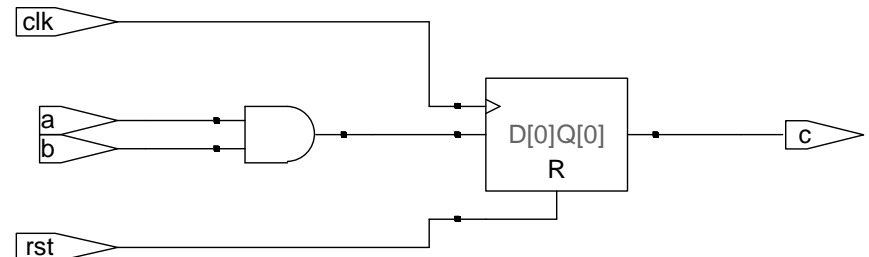
```
always @ (posedge clk, posedge rst)
if (rst)
    c <= 1'b0;
else
    c <= a & b;
```



Always – Flip Flop

- In Xilinx FPGAs
 - Reset and set can be synchronous or asynchronous
 - Priority in synchronous case:
 - reset, set, ce
- Asynchronous example:
 
```
always @ (posedge clk, posedge rst,  
posedge set)  
if (rst)  
    c <= 1'b0;  
else if (set)  
    c <= 1'b1;  
else if (ce)  
    c <= a & b;
```




Always – comb. logic

- Result is continuously calculated – if any of the inputs changes the output immediately changes

```
always @ (a, b)  
c <= a & b;
```


```
always @ (*)  
c <= a & b;
```

 

Always – latch

- Latch: level sensitive storage element
 - as long as the „gate” input is ‘1’, the input is sampled into the latch
 - If the „gate” input is ‘0’, the previously sampled value is kept
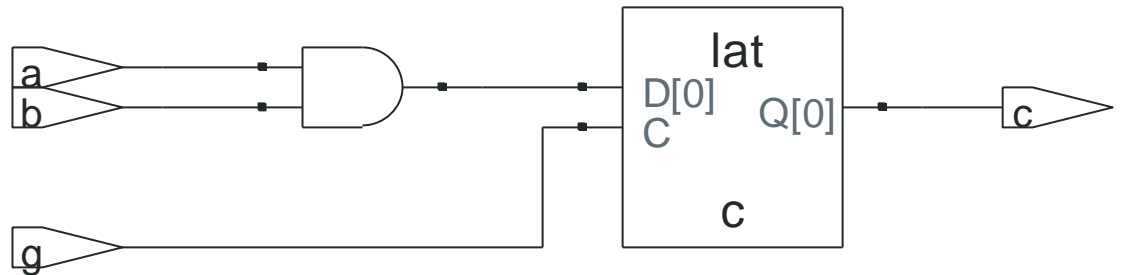
```
always @ (*)  
if (g)  
  c <= a & b;
```




Always – latch error

- Using latch is typically a bad idea; it can be generated by wrong code
 - Not full if or case statements
 - Synthesizers typically give a warning

```
always @ (*)
case (sel)
  2'b00: r <= in0;
  2'b01: r <= in1;
  2'b10: r <= in2;
endcase
```
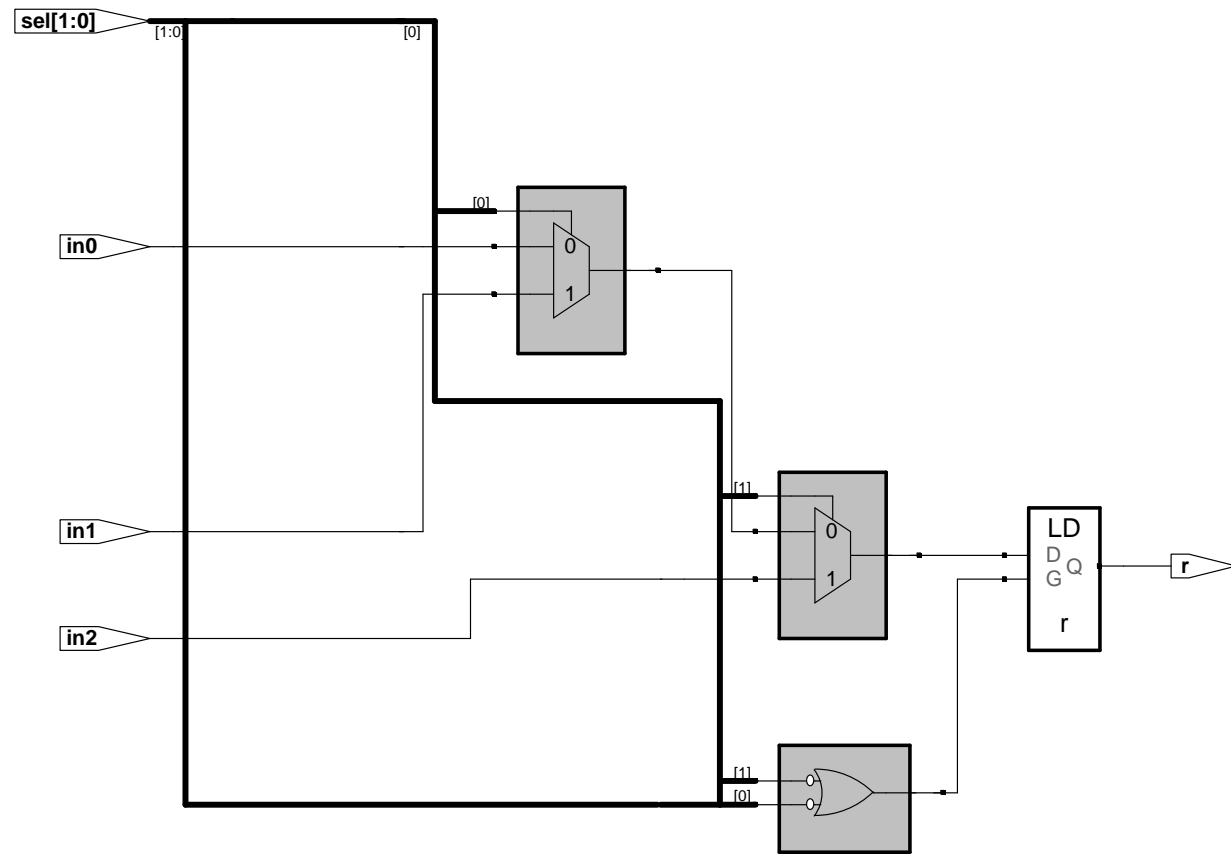
```
always @ (*)
if (sel==0)
  r <= in0;
else if (sel==1)
  r <= in1;
else if (sel==2)
  r <= in2;
```




Always – correct if/case

- Correct code using combinatorial if/case

```
always @ (*)
case (sel)
  2'b00: r <= in0;
  2'b01: r <= in1;
  2'b10: r <= in2;
  default: r <= 'bx;
endcase
```
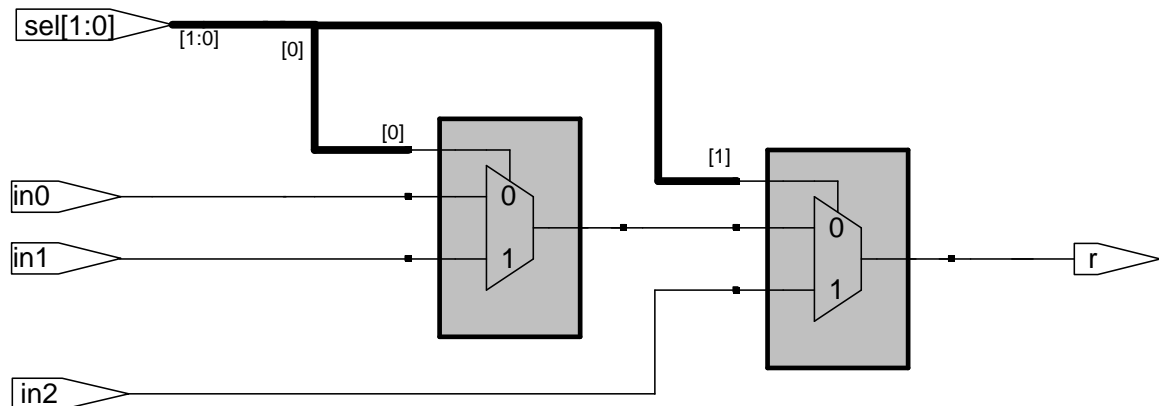
```
always @ (*)
if (sel==0)
  r <= in0;
else if (sel==1)
  r <= in1;
else
  r <= in2;
```




Structural description

- Creating hierarchy: connecting modules

```
module top_level (input in0, in1, in2, output r);  
  
    wire xor0;  
    xor_m xor_inst0(.i0(in0), .i1(in1), .o(xor0));  
    xor_m xor_inst1(.i0(xor0), .i1(in2), .o(r));  
  
endmodule
```

 - Port – signal assignment based on the port names



Example – MUX (1.)

- 2:1 multiplexer

```
module mux_21 (input in0, in1, sel, output r);  
assign r = (sel==1'b1) ? in1 : in0;  
endmodule
```


```
module mux_21 (input in0, in1, sel, output reg r);  
always @ (*)  
if (sel==1'b1) r <= in1;  
else          r <= in0;  
endmodule
```

```
module mux_21 (input in0, in1, sel, output reg r);  
always @ (*)  
case(sel)  
    1'b0:    r <= in0;  
    1'b1:    r <= in1;  
endmodule
```

Example – MUX (2.)

 - 4:1 multiplexer

```
module mux_41 (input in0, in1, in2, in3, input [1:0] sel, output reg r);  
always @ (*)  
case(sel)  
    2'b00: r <= in0;  
    2'b01: r <= in1;  
    2'b10: r <= in2;  
    2'b11: r <= in3;  
endcase  
endmodule
```



Example – Shift register

- 16 bit deep shift register (e.g. for delaying a value)

```
module shr (input clk, sh, din, output dout);
```

```
reg [15:0] shr;
```

```
always @ (posedge clk)
```

```
if (sh)
```

```
shr <= {shr[14:0], din};
```

```
assign dout = shr[15];
```

```
endmodule
```

Example – Counter

- Binary counter with synchronous reset, clock enable, load and direction inputs

```
module m_cntr (input      clk, rst, ce, load, dir,
               input [7:0] din,
               output [7:0] dout);

    reg [7:0] cntr_reg;
    always @ (posedge clk)
    if (rst)
        cntr_reg <= 0;
    else if (ce)
        if (load)
            cntr_reg <= din;
        else if (dir)
            cntr_reg <= cntr_reg - 1;
        else
            cntr_reg <= cntr_reg + 1;

    assign dout = cntr_reg;

endmodule
```

Example – Secundum counter

- 50 MHz clock frequency, 1 sec = 50 000 000 clocks

```
module sec (input clk, rst, output [6:0] dout);
```

```
reg [25:0] clk_div;
```

```
wire tc;
```

```
always @ (posedge clk)
```

```
if (rst)
```

```
    clk_div <= 0;
```

```
else
```

```
    if (tc)
```

```
        clk_div <= 0;
```

```
    else
```

```
        clk_div <= clk_div + 1;
```

```
assign tc = (clk_div == 49999999);
```

```
reg [6:0] sec_cntr;
```

```
always @ (posedge clk)
```

```
if (rst)
```

```
    sec_cntr <= 0;
```

```
else if (tc)
```

```
    if (sec_cntr==59)
```

```
        sec_cntr <= 0;
```

```
    else
```

```
        sec_cntr <= sec_cntr + 1;
```

```
assign dout = sec_cntr;
```

```
endmodule
```

Tri-state lines


- Bi-directional buses, eg.
 - E.g. data bus of external memories

```
module tri_state (input clk, inout [7:0] data_io);  
  
wire [7:0] data_in, data_out;  
wire bus_drv;  
  
assign data_in = data_io;  
assign data_io = (bus_drv) ? data_out : 8'bz;  
  
endmodule
```

- The bus drive enable signal is critical (bus_drv), take care when generating it

FSM – Finite State Machine

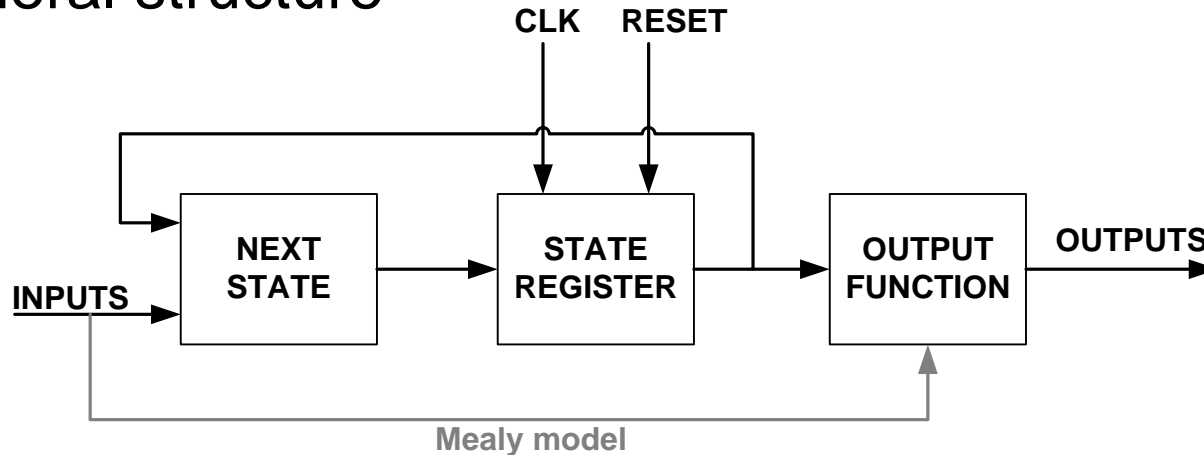
- FSM – to create complex control machines
- General structure



- State register: state variable
- Next state function: determines the next state (combinatorial logic)
- Output function: generates outputs
 - Moore: based on the state register
 - Mealy: based on the state registers and the current inputs

FSM example

 - Traffic light (simple)
 - States: red, yellow, green, red-yellow (no blinking yellow)
 - Inputs: timers for the different states
 - Output: state



FSM example – Verilog (1)

```
module light(  
    input          clk, rst,  
    output reg [2:0] led);  
  
parameter RED     = 2'b00;  
parameter RY     = 2'b01;  
parameter GREEN  = 2'b10;  
parameter YELLOW = 2'b11;  
  
reg [15:0] timer;  
reg [1:0] state_reg;  
reg [1:0] next_state;  
  
always @ (posedge clk)  
if (rst)  
    state_reg <= RED;  
else  
    state_reg <= next_state;
```

```
always @ (*)  
case(state_reg)  
    RED: begin  
        if (timer == 0)  
            next_state <= RY;  
        else  
            next_state <= R;  
        end  
    RY: begin  
        if (timer == 0)  
            next_state <= GREEN;  
        else  
            next_state <= RY;  
        end  
    YELLOW: begin  
        if (timer == 0)  
            next_state <= RED;  
        else  
            next_state <= YELLOW;  
        end  
    GREEN: begin  
        if (timer == 0)  
            next_state <= YELLOW;  
        else  
            next_state <= GREEN;  
        end  
    default:  
        next_state <= 3'bxxx;  
endcase
```

FSM example – Verilog (2)

```
always @ (posedge clk)
case(state_reg)
  RED: begin
    if (timer == 0)
      timer <= 500;    //next_state <= RY;
    else
      timer <= timer - 1;
    end
  RY: begin
    if (timer == 0)
      timer <= 4000;  //next_state <= GREEN;
    else
      timer <= timer - 1;
    end
  YELLOW: begin
    if (timer == 0)
      timer <= 4500;  //next_state <= RED;
    else
      timer <= timer - 1;
    end
  GREEN: begin
    if (timer == 0)
      timer <= 500;    //next_state <= YELLOW;
    else
      timer <= timer - 1;
    end
endcase
```

- Timer
 - Loads a new value when state changes
 - Down-counter
 - ==0: state change

```
always @ (*)
case (state_reg)
  RY :      led <= 3'b110;
  RED:     led <= 3'b100;
  YELLOW:  led <= 3'b010;
  GREEN:   led <= 3'b001;
  default: led <= 3'b100;
endcase

endmodule
```


Simulation

- Testbench creation: drive the input ports of the unit under test
 - Verilog Test Fixture
 - Generating inputs using Verilog
 - All synthesizable language elements can be used
 - Other constructs which are not synthesizable are also available (e.g. delay)
- Simulator
 - ISE Simulator (Isim)
 - Modelsim (MXE)


Verilog Test Fixture

- Test Fixture
 - Test Fixture is a Verilog module
 - The module under test is a sub-module of the test fixture
 - All Verilog syntax constructs can be used
 - There are non-synthesizable constructs
- Time base
 - `'timescale 1ns/1ps`
 - Time base is 1 ns
 - Simulation resolution: 1 ps

Test Fixture - initial

- „initial” block
 - Execution starts at time „0”
 - Executed once
 - „initial” blocks are executed in parallel with each other and with always blocks and assigns
- The delays are cumulative, e.g.
 
```
initial  
begin  
  a <= 0;  
  #10 a <= 1;  
  #25 a <= 2;  
  #5  a <= 0;  
end
```




Test Fixture - always

- Generating clock

```
initial  
  clk <= 1;  
  
always #5  
  clk <= ~clk;
```

- Clocked inputs (propagation time!)
 
```
initial cctr <= 0;  
always @ (posedge clk)  
  #2 cctr <= cctr + 1;
```




Task

- Declaration:
 - In the module which uses the task
 - In a different file (more modules can use the same task)
- Arbitrary number of inputs and outputs
- Can contain timing (delay)
- Variables declared in a task are local variables
- Global variables can be read or written by the task
- A task can call another task

 Example - Task

- Simulating an asynchronous read operation



- Verilog code

```
task bus_w(input [15:0] addr, input [7:0] data);
begin
    xaddr <= addr;
    #5 xdata <= data;
    #3 xwe <= 0;
    #10 xwe <= 1;
    while (xack != 1) wait;
    #4 xdata <= 8'bz;
    xaddr <= 0;
end
endtask;
```

Example - Task

- „bus_w” is located in „tasks.v” file
- x* variables used by the task are global variables defined in the test fixture
- Using the task in a test fixture
 - 3 write cycles
 - 10 ns between them

```
`include "tasks.v"  
  
initial  
begin  
    bus_w(16'h0, 8'h4);  
    #10 bus_w(16'h1, 8'h65);  
    #10 bus_w(16'h2, 8'h42);  
end
```

File operations

- Reading data into an array

```
reg [9:0] input_data[255:0];  
initial  
    $readmemh("input.txt", input_data);
```

- Writing data into a file

```
integer file_out;  
wire res_valid;  
wire [16:0] res;  
  
initial  
    file_out = $fopen("output.txt");  
  
always @ (posedge clk)  
if (out_valid)  
    $fwrite(file_out, "%d \n", res);
```