

$$A 1.) \hat{W} = \frac{1}{N_1} \sum_{i=1}^{N_1} W_i = 123,96 \text{ kWh} \quad (N_1=5)$$

$$s = \sqrt{\frac{1}{N_1-1} \sum_{i=1}^{N_1} (W_i - \hat{W})^2} = 8,3512 \text{ kWh} \quad (1)$$

$$\Delta W = \frac{s}{\sqrt{N_1}} \cdot t_{4,0,995} = 17,161 \text{ kWh}$$

4,595


$$P[\hat{W} - \Delta W < W < \hat{W} + \Delta W] = 1 - b \quad b = 0,01$$

$$P[106,8 \text{ kWh} < W < 141,1 \text{ kWh}] = 99\%$$

5

2

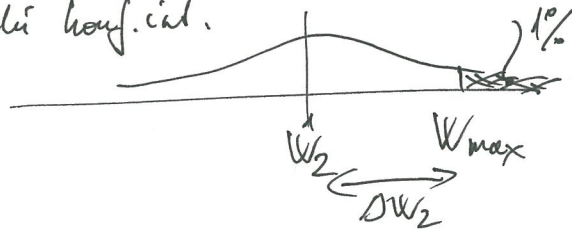Maximális fogyasztás: egyoldali konf. int.



$$\hat{W}_2 = N_2 \cdot W_1 = 31,2 \text{ MWh} \quad (N_2 = 5 \cdot 52 = 260)$$

$$\Delta W_2 = \sqrt{N_2} \cdot s_1 \cdot z_{0,99} = 144,5 \text{ kWh}$$

Student \rightarrow norm.
(C.K.T.)

$$W_{\max} = \hat{W}_2 + \Delta W_2 = 31,346 \text{ MWh}$$

$$A 11.) \frac{R_x + j\omega L_x}{R_3} = R_2 Y_4 = R_2 (G_4 + j\omega C_4)$$

$$R_x = \frac{R_2 R_3}{R_4} = 7,8125 \Omega$$

$$L_x = R_2 R_3 C_4 = 375 \text{ mH}$$

2

$$\frac{1}{R_p} + \frac{1}{j\omega L_p} = \frac{1}{R_x + j\omega L_x} \Rightarrow$$

$$R_p = \frac{R_x^2 + \omega^2 L_x^2}{R_x} = 2569 \Omega$$

$$L_p = \frac{R_x^2 + \omega^2 L_x^2}{\omega^2 L_x} = 376,7 \text{ mH}$$

2

$$\frac{\Delta R_x}{R_x} = 3 \cdot 0,1\% = 0,3\%$$

1

$$\frac{\Delta L_x}{L_x} = 2 \cdot 0,1\% + 0,3\% = 0,5\%$$

5